# IMPLEMENTATION OF BOOLEAN LOGIC IN AVR-GCC

### V.GOKULKUMAR

velicharlagokulkumar@gmail.com
FWC22034 IITH Future Wireless Communication (FWC)

ASSIGN-3

### **Contents**

1	Con	nponents	1
2	2.1 2.2	lementation  METHOD-1  METHOD-2  METHOD-3	1

X	Y	Z	F	
0	0	0	1	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	1	

Table-1

## **Abstract**

To Obtain the Boolean Expression for the Logic circuit shown below

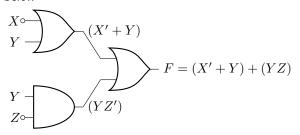


Fig. 1

## 2.2 METHOD-2

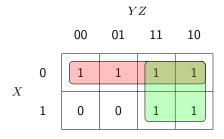


Fig. 2

**Karnugh Map :** The expression in (2.1) can be minimized using the K-map in Fig 2. In Fig.2, the implicants in boxes 0,1,2,3 result in X' The implicants in boxes 2,3,6,7 result in Y Thus, after minimization using Fig. 2, (2.1) can be expressed as F=X'+Y......(2.2). Verify the truth table for F in TABLE 1. The code below realizes the Boolean logic for F in 2.2

https://github.com/velicharlagokulkumar/FWC\_module1/blob/main/avr-gcc/codes/method\_2/main.c

# 1 Components

Components	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	5
Breadboard		1

# 2 Implementation

#### 2.1 METHOD-1

The truth table for Fig. 1 is available in Table-1 Using Boolean logic, output F in Table 1 can be expressed in terms of the inputs X, Y, Z as F=(X'+Y)+(Y.Z').....(2.1) Built in led at 13th pin of Arduino will glow for the logic '1' of F based on the initialization of X,Y,Z. The code below realizes the Boolean logic for F in Table-1

https://github.com/velicharlagokulkumar/FWC\_module1/blob/main/avr-gcc/codes/method\_1/main.c

#### ubuntu command line commands

l 1	_				
make	.tor	running	and	flashing	

#### 2.3 METHOD-3

The code below realizes the Boolean logic for F in (2.2) using 5V,GND of Arduino

D3,D4,D5 Pins of Arduino are configured as input pins instead of initializing X,Y,Z inside software,inputs are given manually as X,Y,Z.Built in led will glow based on F satisfying the Table-1

https://github.com/velicharlagokulkumar/FWC\_module1/blob/main/avr-gcc/codes/method\_3/main.c