# IMPLEMENTATION OF BOOLEAN LOGIC IN IDE

## V.GOKULKUMAR

velicharlagokulkumar@gmail.com IITH Future Wireless Communication (FWC) FWC22034

ASSIGN-1

# **Contents**

| 1 | 1 Components |  |  |   |  |  |
|---|--------------|--|--|---|--|--|
| 2 | 2.1<br>2.2   | olementation  METHOD-1  METHOD-2  METHOD-3 |  | 1 |  |  |

#### X 7 F 0 0 0 1 0 0 1 1 0 0 1 1 0 1 1 1 1 0 0 0 0 0 1 1 1 1 0 1 1 1 1

Table-1

# **Abstract**

To Obtain the Boolean Expression for the Logic circuit shown below

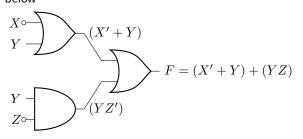


Fig. 1

#### 2.2 METHOD-2

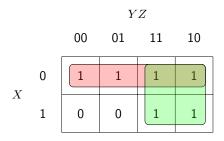


Fig. 2

### Components 1

| Components  | Values | Quantity |
|-------------|--------|----------|
| Arduino     | UNO    | 1        |
| JumperWires | M-M    | 5        |
| Breadboard  |        | 1        |

**Karnugh Map:** The expression in (2.1) can be minimized using the K-map in Fig 2. In Fig.2 ,the implicants in boxes 0,1,2,3 result in X' The implicants in boxes 2,3,6,7 result in Y Thus, after minimization using Fig. 2, (2.1) can be expressed as F=X'+Y.....(2.2). Verify the truth table for F in TABLE 1. The code below realizes the Boolean logic for F in 2.2

https://github.com/velicharlagokulkumar/FWC\_module1/ tree/main/Assignment-1/IDE/codes/method\_2/src/ method\_2.cpp

### 2 **Implementation**

#### 2.1 METHOD-1

The truth table for Fig. 1 is available in Table-1 Using Boolean logic, output F in Table 1 can be expressed in terms of the inputs X, Y, Z as F=(X'+Y)+(Y.Z')....(2.1)Built in led at 13th pin of Arduino will glow for the logic '1' of F based on the initialization of X,Y,Z. The code below realizes the Boolean logic for F in Table-1

https://github.com/velicharlagokulkumar/FWC\_module1/ tree/main/Assignment-1/IDE/codes/method\_1/src/ method\_1.cpp

5V,GND of Arduino

METHOD-3

D3,D4,D5 Pins of Arduino are configured as input pins instead of initializing X,Y,Z inside software,inputs are given manually as X,Y,Z.Built in led will glow based on F satisfying the Table-1

The code below realizes the Boolean logic for F in (2.2) using

https://github.com/velicharlagokulkumar/FWC\_module1/ tree/main/Assignment-1/IDE/codes/method\_3/src/ method\_3.cpp

## ubuntu command line commands

| pio runfor                   | running       |
|------------------------------|---------------|
| pio run —t nobuild —t upload | .for flashing |